

R1 APPEARS TO BE BRN-ORG-BLK-ORG-SILVER = 130K

FLAT ROUND MAGNET BELOW COIL. SMALL STEEL CYLINDRICAL POLE PIECE IN CENTER OF WINDINGS (BOTH COILS)


ESTIMATED COIL SPECS:

INPUT COIL
 DC RESISTANCE: 600 OHMS (?)
 INDUCTANCE: 45-50mH
 WIRE: 46 AWG / 0.04mm DIAMETER
 APPROX. 3000 TURNS

OUTPUT COIL
 DC RESISTANCE: 16-32 OHMS (?)
 INDUCTANCE: 2-3mH
 WIRE: 36 AWG / 0.12MM DIAMETER
 APPROX. 300 TURNS?

DIAMETER OF BOTH WINDINGS IS APPROX. 9.3mm



PCB (VIEW FROM GUITAR STRING SIDE)

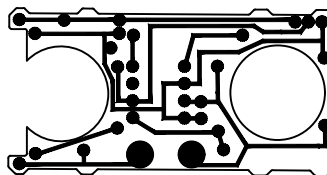

PCB (FOIL SIDE)
 ACTUAL SIZE



Ebow Circuit Board

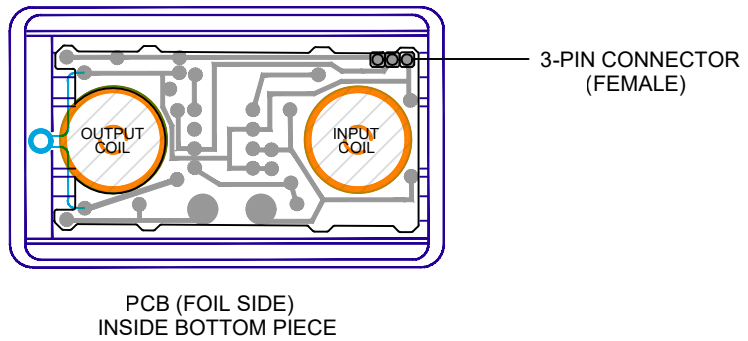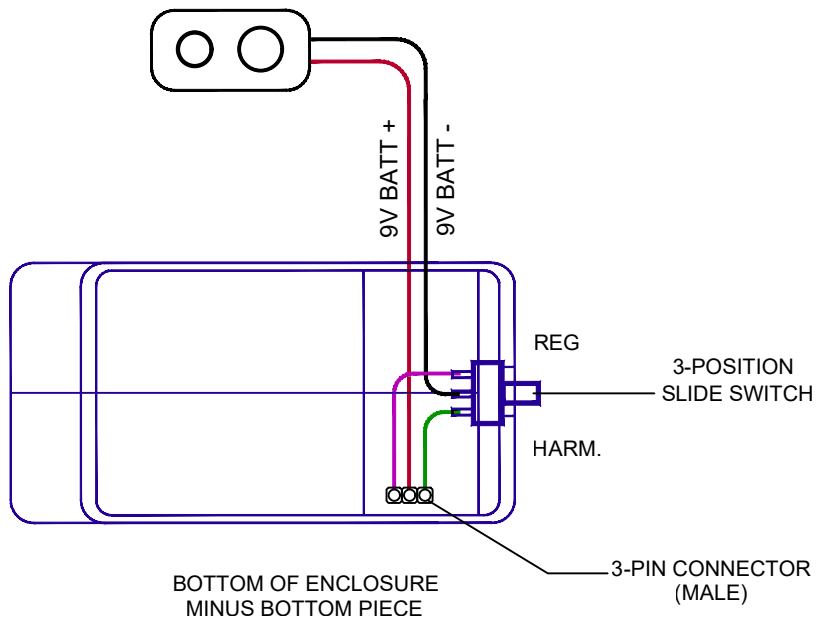Device Designed by Gregory S. Heet
 Drawn & Verified by Paul Marossy 12/10/2022




Ebow Switch Wiring

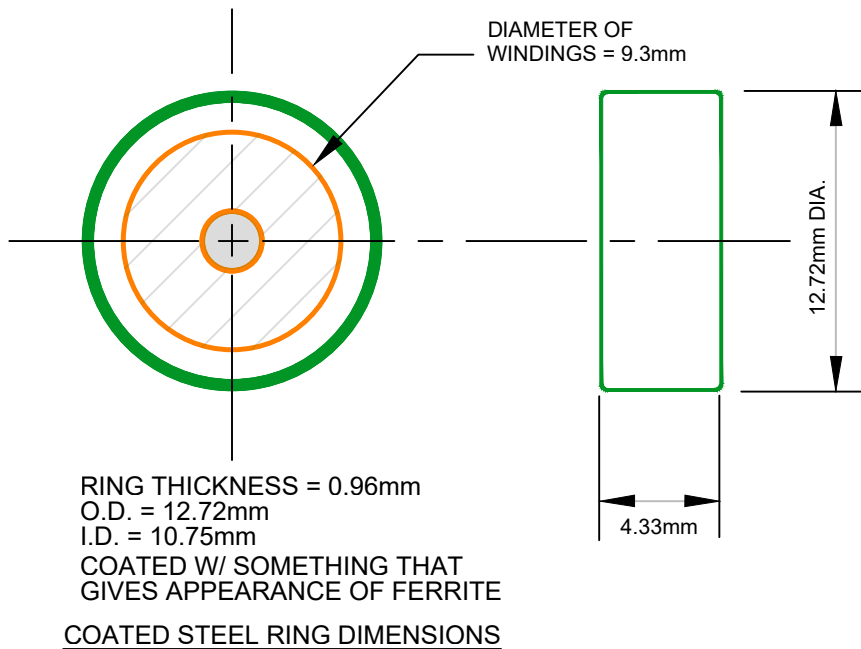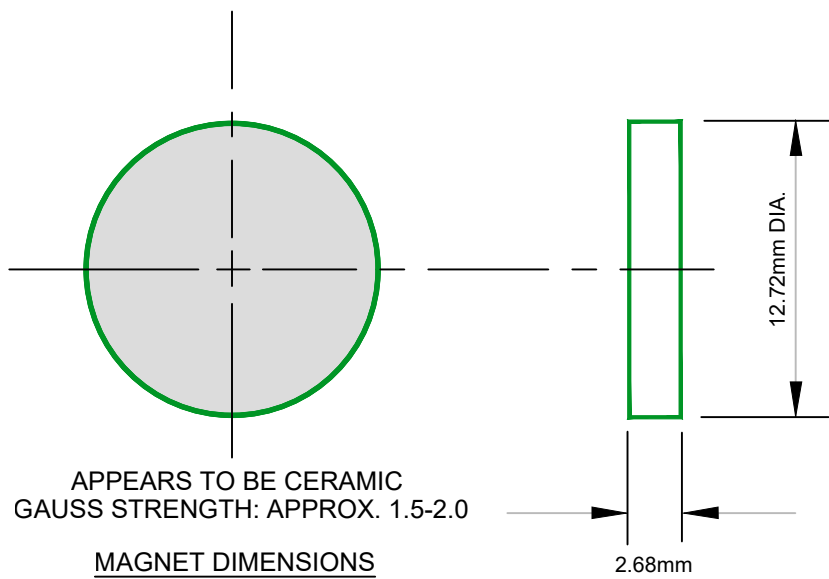Device Designed by Gregory S. Heet
 Drawn & Verified by Paul Marossy 12/10/2022




Ebow Magnet & Core Data

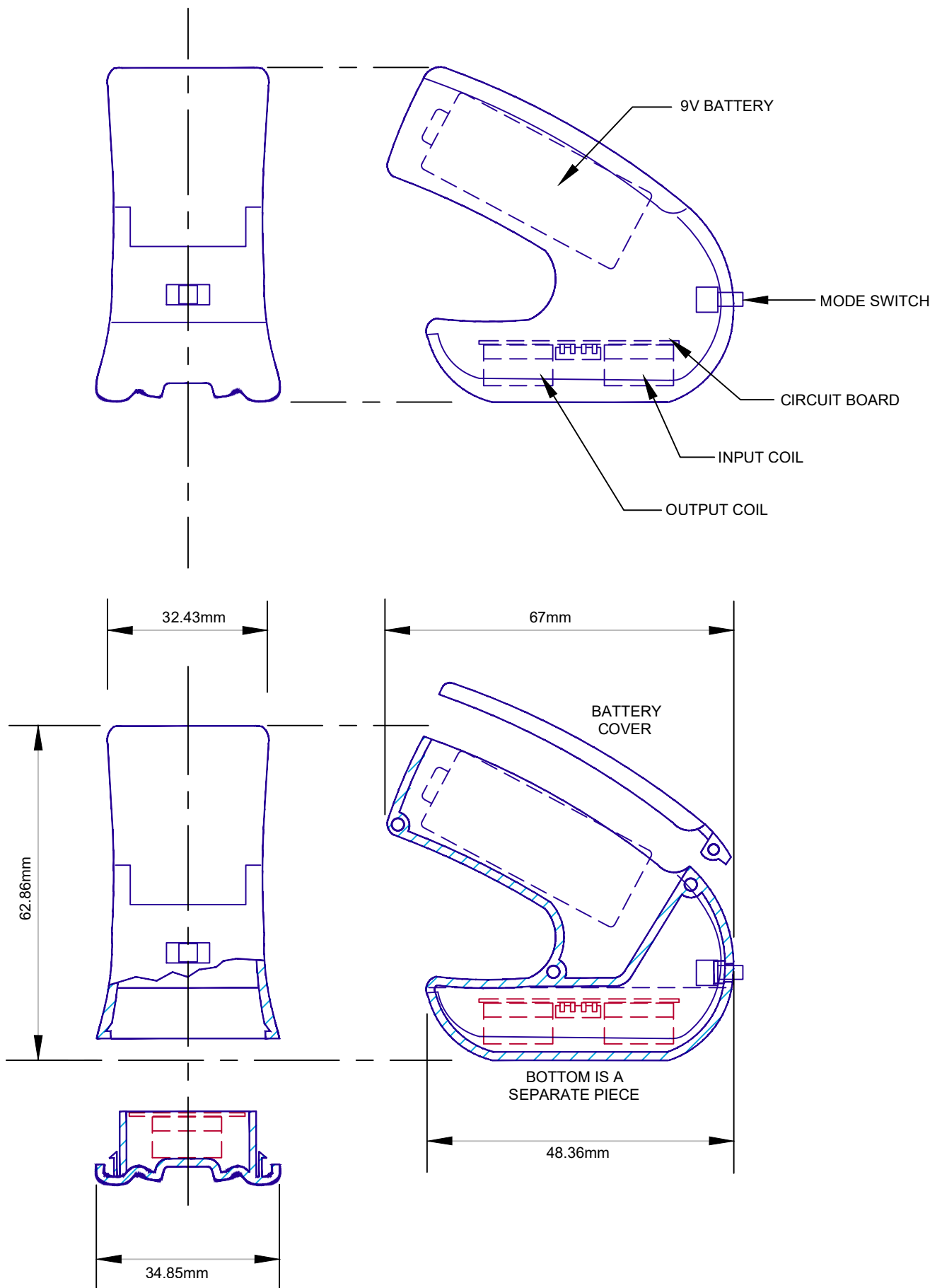Device Designed by Gregory S. Heet
Drawn & Verified by Paul Marossy 12/10/2022




Ebow Plastic Enclosure

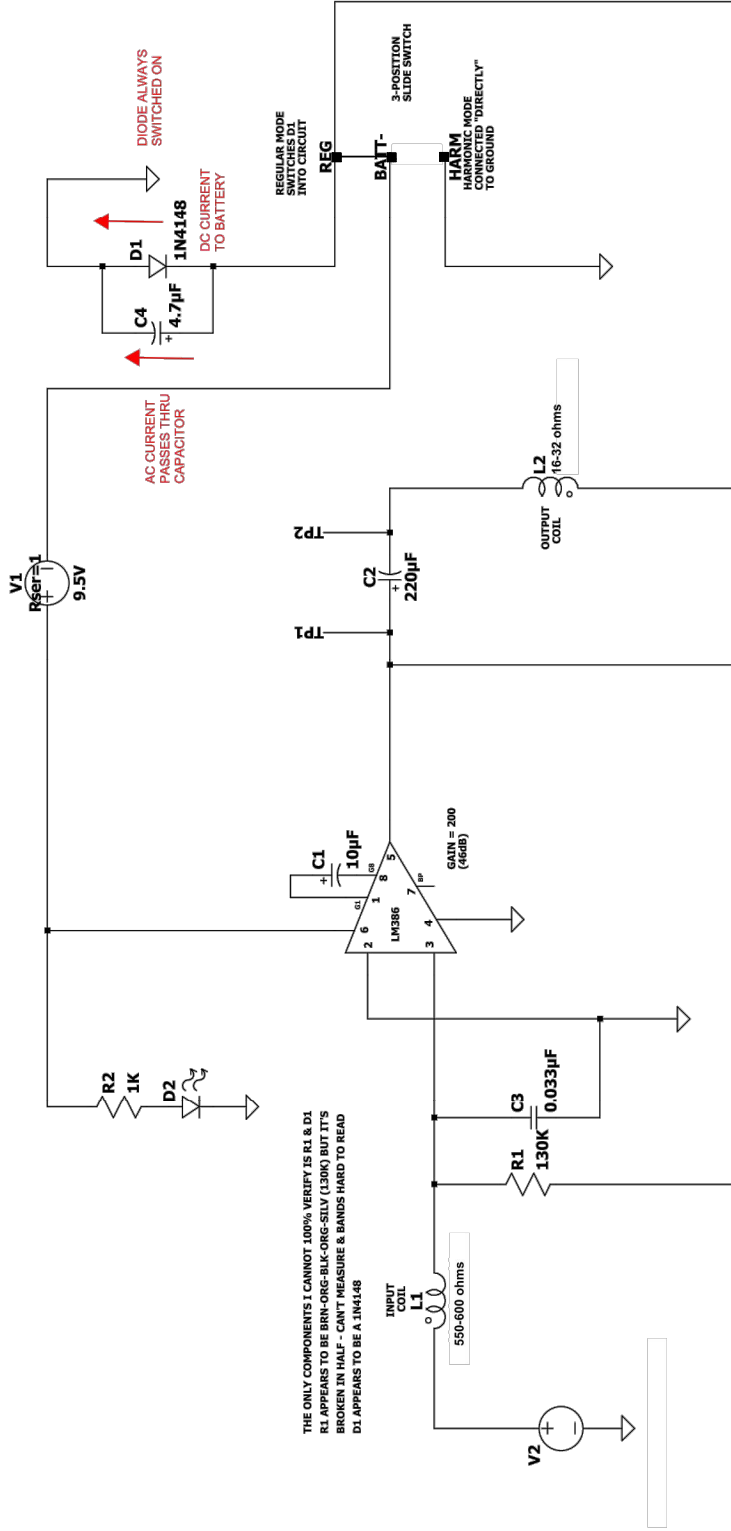Device Designed by Gregory S. Heet
 Drawn & Verified by Paul Marossy 12/10/2022



THE ONLY COMPONENTS I CANNOT VERIFY IS R1 & D1
 R1 APPEARS TO BE BRN-ORG-BLK-ORG-SILV (130K) BUT IT'S
 BROKEN IN HALF - CANT MEASURE & BANDS HARD TO READ
 D1 APPEARS TO BE A 1N4148

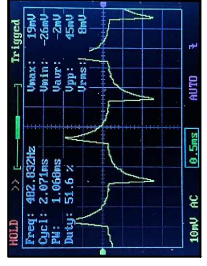
PER PATENT DOCUMENTS: (IN HARMONIC MODE)
 THE DIODE IS SWITCHED OFF AND THE CURRENT
 REVERSED, WHICH HAS THE EFFECT OF DAMPING THE
 FUNDAMENTAL FREQUENCY AND THE HARMONICS AND
 OVERTONES ARE DRIVE INSTEAD



Ebw Schematic

NORMAL MODE

WAVE FORM AT PICKUP OUT

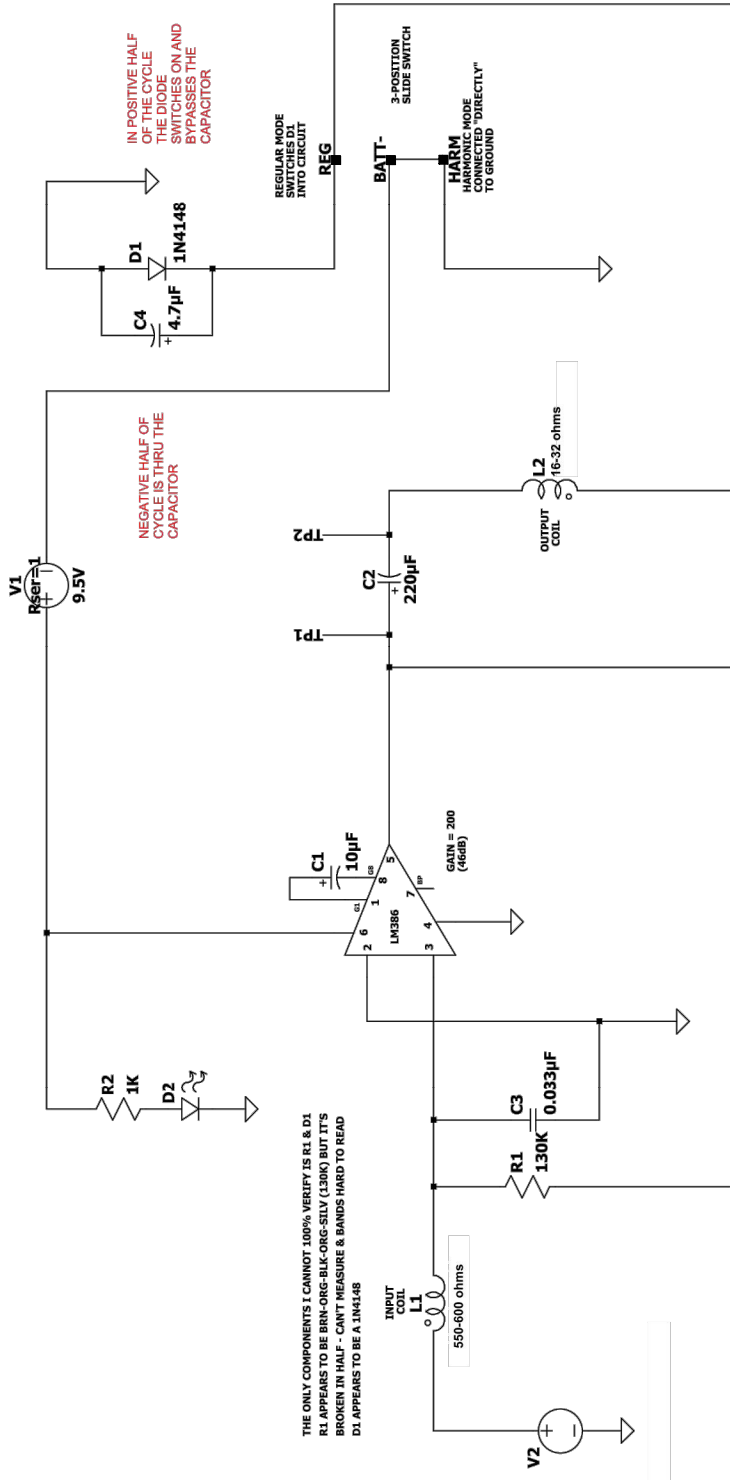


WHEN THE WAVE FORM IS NEGATIVE, THE 4.7µF CAPACITOR INTRODUCES AN RC HIGH PASS FILTER (ACTUALLY RLC IF YOU INCLUDE THE DRIVER COIL INDUCTANCE). IF THE OUTPUT OF THE DRIVER COIL IS POSITIVE, THE CAPACITOR IS BYPASSED BY THE DIODE. THE OUTPUT OF THE DRIVER COIL WILL LOOK LIKE A CURVED SAWTOOTH AND THE POWER WILL BE REDUCED IN THE DRIVER COIL.*

* HOWEVER, IN REAL WORLD TESTING, THE HARMONIC MODE HAS A HIGHER OUTPUT AT THE PICKUP OUT

PER PATENT DOCUMENTS: (IN HARMONIC MODE) THE EFFECT OF DAMPING THE FUNDAMENTAL FREQUENCY AND THE HARMONICS AND OVERTONES ARE DRIVE INSTEAD

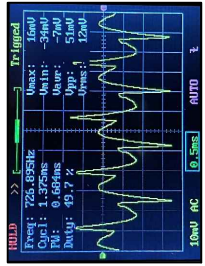
THE ONLY COMPONENTS I CANNOT VERIFY IS R1 & D1 R1 APPEARS TO BE BRN-ORG-BLK-ORG-SILV (130K) BUT IT'S BROKEN IN HALF - CANT MEASURE & BANDS HARD TO READ D1 APPEARS TO BE A 1N4148




WAVE FORM AT PICKUP OUT

Ebw Schematic


HARMONIC MODE

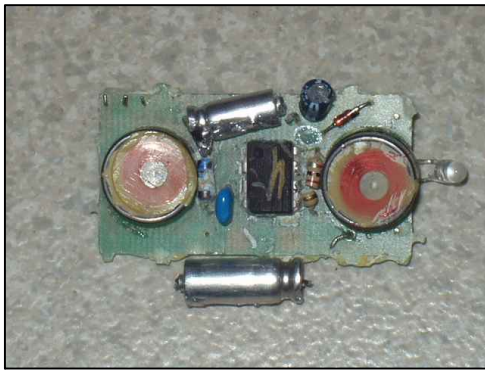


EXAMPLE #1: PCB COMPONENT SIDE

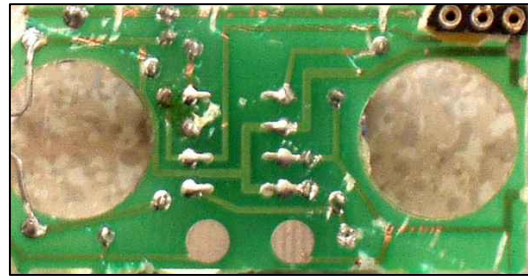


EXAMPLE #1 PCB FOIL SIDE

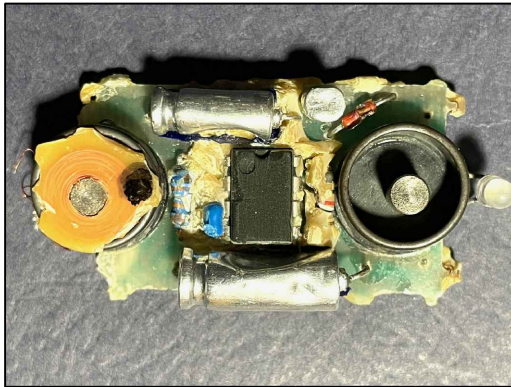


EXAMPLE #2: PCB COMPONENT SIDE

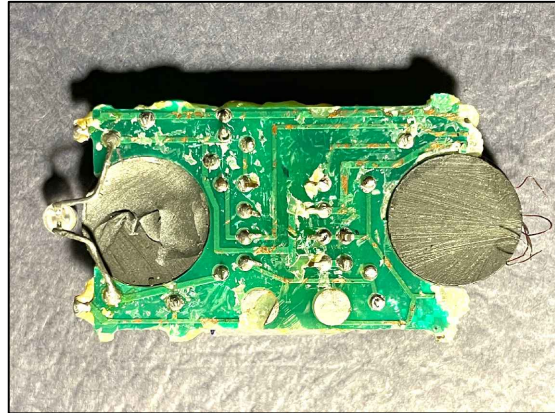

EXAMPLE #2 PCB FOIL SIDE

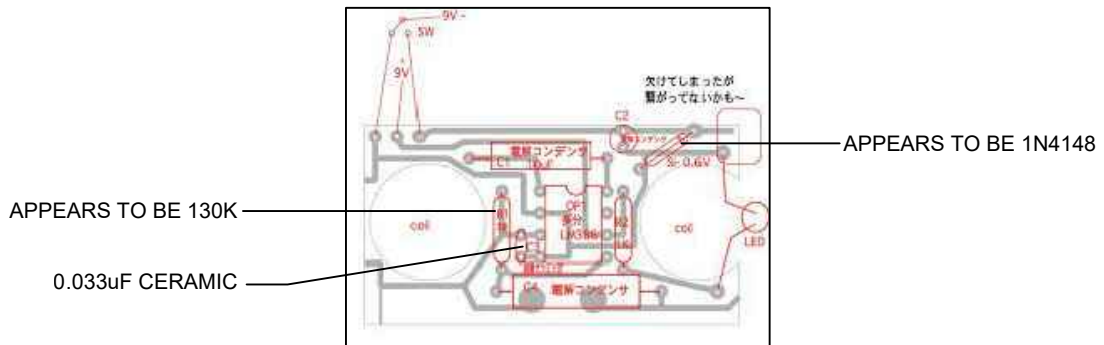

PCB COMPONENT SIDE

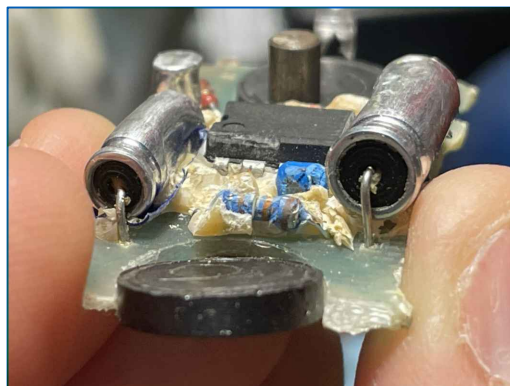

CLOSE UP OF R1. APPEARS TO BE BRN-ORG-BLK-ORG-SLV 130K