
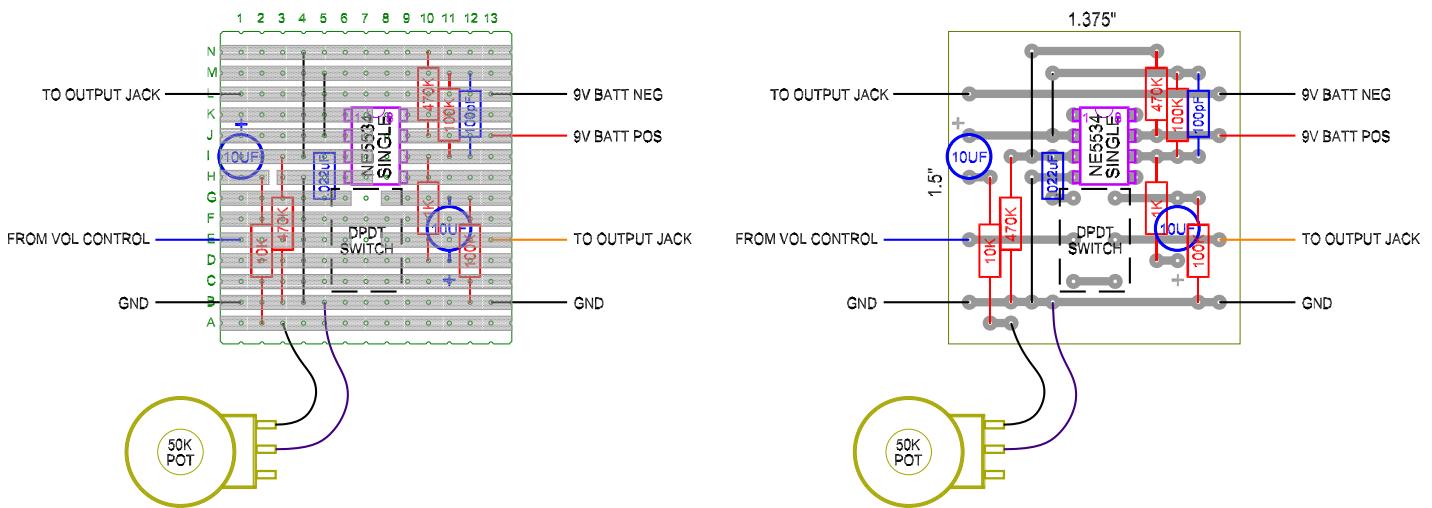


Notes:

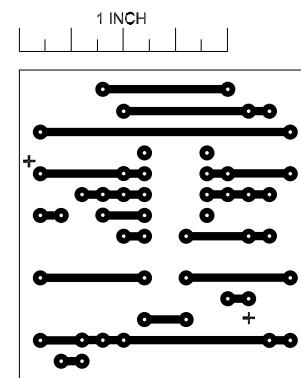1. Pot is suggested to be a linear 20-turn precision type, but a regular pot could also be used.
2. A high performance single opamp is recommended. TL071 is suggested in book. The Burr-Brown OP134A also works well in this circuit.
3. On veroboard layout, cut copper tracks at E7, G7, H3, H8, I8, J8 & K8.



Veroboard Layout

PCB Layout